

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

B.Tech
PME5H006

5th Semester Regular Examination 2017-18
Analog & Digital Electronics
BRANCH: MECH
Time: 3 Hours
Max Marks: 100
Q.CODE: B496


Answer Question No.1 and 2 which are compulsory and any four from the rest.
The figures in the right hand margin indicate marks.

Q1 Answer the following questions: *multiple type or dash fill up type* (2 x 10)


- a) Emission coefficient of Germanium is
- b) What is mean by PIV rating of a diode
 - a) Maximum reverse bias potential which can be applied across a diode without breakdown
 - b) Maximum forward bias potential which can be applied across a diode without breakdown
 - c) Minimum potential required by a diode to reach conduction state
 - d) Maximum power allowable to a diode
- c) When temperature increases reverse saturation current
- d) MOSFET can be used as a
 - A. current controlled capacitor
 - B. voltage controlled capacitor
 - C. current controlled inductor
 - D. voltage controlled inductors
- e) Which of the following is not associated with a p-n junction
 - A.junction capacitance
 - B.charge storage capacitance
 - C.depletion capacitance
 - D.channel length modulation
- f) The cascade amplifier is a multistage configuration of
- g) SR Flip flop can be converted to T-type flip-flop if
- h) The load impedance Z_L of a CE amplifier has R and L in series. The phase difference between output and input will be
- i) The Gray code for decimal number 6 is equivalent to
- j) The decimal equivalent of 10010111 is ----

Q2 Answer the following questions : (2 x 10)

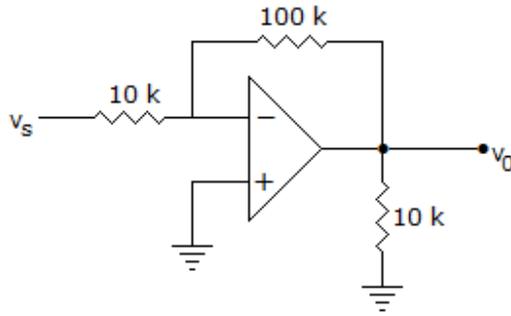- a) What is difference between latch and flip-flop?
- b) What is barkhausen criterion ?
- c) The Boolean expression $A.B + A.B + A.B$ is equivalent to .
- d) Derive the Shockley's equation.
- e) What is common collector configuration of BJT ?
- f) What is the use of state diagram?
- g) A half wave diode circuit using ideal diode has an input voltage $20 \sin \omega t$ volts. Calculate the average and rms values of output voltage .
- h) Define race around condition.
- i) The input impedance of op-amp circuit of figure is



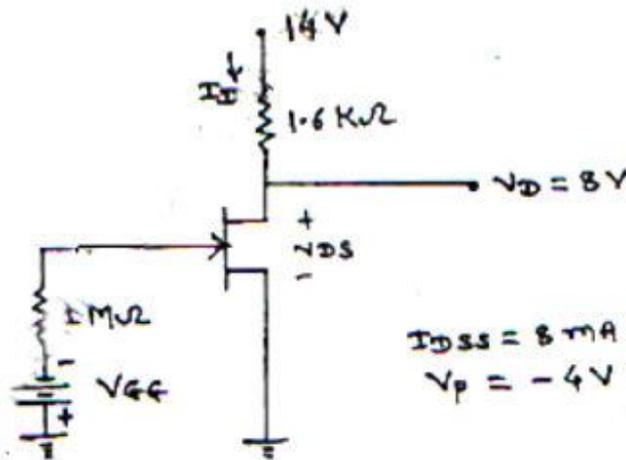- j) A CB amplifier has $r_e = 6 \Omega$, $R_L = 600 \Omega$ and $a = 0.98$. Find the voltage gain .
- Q3** a) Draw the circuit for voltage divider configuration for BJT. (10)
 a. Also derive the expression for the operating point.
 b) Write the differences between BJT and FET. (5)
- Q4** a) For the circuit given below find I_D , V_{DS} , V_{GG} (10)



- b) Write down current equation of diode and explain significance of each parameters. (5)
- Q5** a) Mention the types of feedback connections. Draw their block diagrams indicating input and output signal. (10)
 b) List the general characteristics of a negative feedback amplifier and write its advantages. (5)
- Q6** a) Convert the following to other canonical form. (10)
 i) $F(A,B,C,D) = \Sigma(0,2,6,11,13,14)$
 ii) $F(x,y,z) = \Pi(0,1,2,3,4,6,12)$
 b) Obtain Truth table for function $F = xy + xy' + y'z$. (5)
- Q7** a) Configure 16 to 1 MUX using 4 to 1 MUX (10)
 b) Implement XOR gate using NAND gate . (5)
- Q8** a) Define slew rate of Op-Amp. (ii) Determine the cutoff frequency of OP-amp whose unity gain bandwidth is 1 MHz and open loop gain is 2×10^5 . (iii) List the expression for the output of non-inverting amplifier and inverting op-amp amplifier (10)
 b) What is differences b/w ideal and practical op-amp amplifier? (5)
- Q9** a) State and prove Demorgan's laws (10)
 b) Explain carry look ahead generator. (5)