

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

M.Sc.  
16MPYC205

**2<sup>nd</sup> Semester Back Examination 2017-18**  
**ELECTRONICS**  
**BRANCH : M.Sc.(AP)**  
**Time : 3 Hours**  
**Max Marks : 70**  
**Q.CODE : C1044**

**Answer Question No.1 which is compulsory and any five from the rest.**  
**The figures in the right hand margin indicate marks.**  
**Answer all parts of a question at a place.**

- Q1. Answer the following questions: (2 x 10)**
- a) Convert  $200_{10}$  to binary system.
  - b) Find the frequency of oscillations of a Wien's bridge oscillator with  $R=20K\Omega$  and  $C=100pF$ .
  - c) Draw the block diagram of a typical operational amplifier.
  - d) Which gates are called universal building blocks.
  - e) Draw the logic gate diagram for the following equation  

$$\overline{(A + B)(A + C)(B + C)} = \overline{(A + B)} + \overline{(A + C)} + \overline{(B + C)}$$
  - f) Draw the ideal voltage transfer curve for ideal differential amplifier.
  - g) What is Barkhausen criterion for oscillation.
  - h) Give an example of a truth table using AND gate and OR gate.
  - i) Define multiplexer.
  - j) A signal of r.m.s amplitude of 10volt is applied to the input terminals of a half-wave dipole. Calculate the radiated power if the input impedance of the dipole is  $Z_{in} = 73 + j42$ .
- Q2. a) With a suitable circuit diagram explain the operation of a RC phase shift oscillator. Find the expression for the frequency and condition of oscillation. (7)**
- b) In a crystal oscillator, the electrical equivalent of a crystal is given by  $L=0.5H$ ,  $C=0.05 pF$ ,  $R=2 k\Omega$  and  $C'=10 pF$ . Find the series and parallel frequencies of the crystal. (3)**
- Q3. a) Give the truth table of a JK flip-flop. What are D flip-flop and T flip-flop? How can these flip-flops be constructed using JK flip-flop? (7)**
- b) What is a half-adder? Give its truth table using circuit diagram. (3)**
- Q4. a) Prove the following Boolean expressions. (5)**
- $$(A + C)(\bar{A} + B) = AB + \bar{A}C$$
- $$(A + B)(A + C) = A + BC$$
- b) Simplify the following four variable Boolean function given in sum of product rotation. (5)**
- $$f(A, B, C, D) = \sum(1,2,3,6,8,9,13,14).$$

- Q5. a)** What is a multivibrator? With the help of a labeled circuit diagram describe the operation of an astable multivibrator. **(7)**
- b)** What is CMRR? **(3)**
- Q6. a)** Describe the function of an operational amplifier as (i) inverter, (ii) adder and (iii) integrator. **(6)**
- b)** Derive the expression for voltage gain of differential amplifier by taking a.c analysis. **(4)**
- Q7.** Give a brief idea about different types of antenna. **(10)**
- Q8. Write short answer on any TWO :** **(5 x 2)**
- a)** RS flip-flop
  - b)** De Morgan's theorems
  - c)** Wien's bridge oscillator
  - d)** Optical fiber