

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

M.Sc.I  
FPYC402

4<sup>th</sup> Semester Regular / Back Examination 2017-18  
**ELECTRONICS**  
**BRANCH : M.Sc.I(AP)**  
**Time: 3 Hours**  
**Max Marks : 70**  
**Q.CODE : C694**

**Answer Question No.1 which is compulsory and any five from the rest.**  
**The figures in the right hand margin indicate marks.**  
**Answer all parts of a question at a place.**

- Q1 Answer the following questions: (2 x 10)**
- a) Define operating point of transistor.
  - b) Distinguish between analog and digital signals.
  - c) Show that  $\beta = \frac{\alpha}{1-\alpha}$ .
  - d) Which feedback is used in an oscillator?
  - e) What do you understand by hybrid parameters? What are their dimensions?
  - f) Define the difference between a voltage and a power amplifier.
  - g) What is modulation factor?
  - h) What is the function of filter in rectifier circuit?
  - i) What is Barkhausen criterion?
  - j) Define NOR gate.
- Q2 a) Explain the working of a full wave centre tap rectifier and derive expressions for efficiency and ripple factor. (6)**
- b) Derive the expression for efficiency of half wave rectifier with resistive load. (4)**
- Q3 a) Draw a circuit diagram of a  $\pi$  – section filter used in a full wave rectifier and calculate its ripple factor. (6)**
- b) In a full-wave rectifier circuit, the voltage across the secondary of transformer is 300 V (r.m.s.). Other parameter of rectifier and LC filter connected with it are given below :  $L=10H, C=4\mu F$  and  $f= 50Hz$ , Calculate voltage d.c. and ripple factor. (4)**
- Q4 a) Draw the equivalent circuit of an ideal zener in the breakdown region. And explain how zener diode maintains constant voltage across the load. (5)**
- b) Explain with a neat diagram the operation of push – pull amplifier circuit. (5)**
- Q5 a) Find out the different h- parameters for a linear circuit and draw its equivalent circuit. (5)**
- b) What do you understand by class A, class B and class C amplifier? (5)**
- Q6 a) Hartley and Colpitt's oscillators work on the same principle. Justify. (3)**
- b) Draw a neat diagram to explain operation of Colpitt oscillator and find out its frequency of oscillation. (7)**

- Q7**   **a)** Draw the circuit diagram of two stages R-C coupled amplifier. Explain about its frequency response curve. **(8)**
- b)** Write the difference between negative and positive feedback. **(2)**
- Q8**   **a)** Define amplitude modulation. Derive the voltage equation of an AM modulation. **(6)**
- b)** Explain AND function with a 2- input AND gate. **(4)**