

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 01

M.Sc.I
FPYC805

8th Semester Regular Examination 2018-19

ELECTRONICS

BRANCH : M.Sc.I(AP)

Time : 3 Hours

Max Marks : 70

Q.CODE : F544

Answer Question No.1 which is compulsory and any FIVE from the rest.
The figures in the right hand margin indicate marks.

- Q1 Answer the following questions : (2 x 10)**
- a) How can NOR gate be used as a universal gate?
 - b) What is meant by frequency response and band width for coupled amplifier?
 - c) Determine the output voltage of an OPAMP for input voltages $v_1 = 150 \mu\text{V}$ and $v_2 = 140 \mu\text{V}$. The amplifier has a differential gain $A_d = 4000$ and the CMRR is 100.
 - d) Define Barkhausen condition. What is its significance?
 - e) What are the advantages of negative feedback in an oscillatory circuit?
 - f) Define acceptance angle and give its formulation for an optical fiber.
 - g) State the uses of the key elements of a radio communication system.
 - h) What is meant by boot strapping in FET?
 - i) Simplify the Boolean identity: $AB + AC + B\bar{C}$
 - j) What is meant by noise in amplifiers? How can this be dealt with effectively?
- Q2 a) Describe the working of an OPAMP as an inverting comparator with a positive reference voltage of 1.5 V and with a negative reference voltage of -1.0 V using an input signal with amplitude of 3V. (5)**
- b) Describe the working of an OPAMP as logarithmic amplifier. (5)**
- Q3 a) Using basic logic gates create the XOR gate. Verify the truth table from the circuit. (5)**
- b) Discuss the working of JK flip flop. What are its advantages and disadvantages? (5)**
- Q4 a) With proper circuit diagram find the stability parameters for collector to base bias transistor. How is the Q-point established in this case? (5)**
- b) Discuss the working of an Astablemultivibrator. (5)**
- Q5 a) Derive the h-parameters of a transistor. (5)**
- b) Briefly describe the functioning of the Klystron oscillator. (5)**
- Q6 With the help of suitable circuit diagramsderive the expressions for the voltage gain and phase angle in mid, low and high frequency range for a RC coupled CE amplifier. (10)**
- Q7 Draw the circuit, discuss the working and derive the expression for frequency of a Wien bridge oscillator. (10)**
- Q8 Write short answer on any TWO : (5 x 2)**
- a) With necessary diagram explain the working of super heterodyne receiver used in radio communication.
 - b) Discuss the applications and advantages of optical fibers.
 - c) Describe current series feedback and current shunt feedback.