

Registration No :

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Total Number of Pages : 02

B.Tech
BE2102


1st Semester Back Examination 2017-18
BASIC ELECTRICAL ENGINEERING
BRANCH : AEIE, AERO, AUTO, BIOMED, BIOTECH,
CHEM, CIVIL, CSE, ECE, EEE, EIE, ELECTRICAL, ENV, ETC,
FASHION, FAT, IEE, IT, ITE, MANUFAC, MANUTECH, MARINE, MECH,
METTA, METTAMIN, MINERAL, MINING, MME, PE, PLASTIC, TEXTILE
Time : 3 Hours
Max Marks : 70
Q.CODE : HB975

Answer Question No.1 which is compulsory and any FIVE from the rest.
The figures in the right hand margin indicate marks.

Q1 Answer the following questions : (2 x 10)

- a) Mention the mode of ammeter and voltmeter connection in a circuit?
- b) Distinguish between a Branch and a node of a circuit.
- c) Give the power equation for a star connected system?
- d) Which type of instrument is called as universal instrument?
- e) What is the use of commutator and brush in a d.c machine?
- f) Mention the two types of rotors of an induction motor?
- g) What is the purpose of laminating the core in a transformer?
- h) An alternating voltage is given by $V=230\sin314t$. Calculate i) frequency, ii) maximum value, iii) average value, iv) RMS value.
- i) Mention the expression for reluctance of a magnetic circuit and what is its unit?
- j) How the direction of rotation of dc motor can be changed?

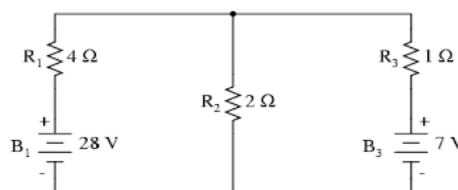Q2 a) Using The venin's Theorem find the current flowing through 2 ohm resistance, as shown in the Fig bellow (5)




- b) An iron ring wound with 550 turn's solenoid produces a fluxdensity of 0.94 tesla in the ring carrying a current of 2.4 Amp. The mean length of iron path is 80 cm and that of air gapis 1 mm. Determine:
 - i) The relative permeability of iron
 - ii) Self-inductance
 - iii) Energy stored in the above arrangement, if the cross sectional area of ring is 25 cms².

Q3 a) Derive the expression for the energy stored in the magnetic field in terms of energy stored per unit volume (5)

- b) What are the factors governing the Value of Resistance? Explain the term Resistivity. (5)

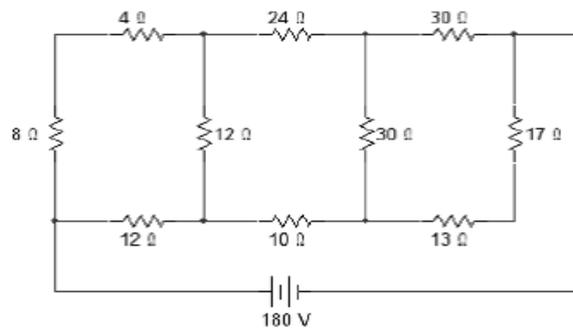- Q4** a) Derive the expression for instantaneous voltage, charge and charging current for a R-C circuit. (5)
b) State and explain Maximum Power Transfer theorem and give one example of application of the theorem. (5)
- Q5** a) Prove that rms value of the sinusoidal alternating current is 0.707 times its maximum value. (5)
b) Compare merits and demerits of moving iron type instruments and dynamometer type instruments. Which one is superior why? (5)
- Q6** a) With a neat circuit diagram Explain the principle of operation of DC Motor. (5)
b) Derive the EMF equation of a transformer. (5)
- Q7** Determine the current in 10Ω resistor in the net work shown, use star-delta conversion. (10)



- Q8** Write short answer on any TWO : (5 x 2)
- a) Residential wiring
 - b) A/D conversion
 - c) Grounding and safety
 - d) PMMC instruments