

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

B.Tech.
PEI4G001

4th Semester Regular Examination 2017-18
DIGITAL ELECTRONIC CIRCUITS
BRANCH : AEIE, EIE, IEE
Time : 3 Hours
Max Marks : 100
Q.CODE : C1154

Answer Part-A which is compulsory and any four from Part-B.
The figures in the right hand margin indicate marks.
Answer all parts of a question at a place.

Part – A (Answer all the questions)

- Q1 Answer the following questions: multiple type or dash fill up type: (2 x 10)
- a) Expansion of PLA is _____
 - b) When two counters are cascaded, the overall MOD number is equal to the _____ of their individual MOD numbers.
 - A. product
 - B. sum
 - C. log
 - D. reciprocal
 - c) A Latch is _____ sensitive.
 - d) In the decimal numbering system, what is the MSD? _____
 - e) Determine the output frequency for a frequency division circuit that contains 12 flip-flops with an input clock frequency of 20.48 MHz.
 - A. 10.24 kHz
 - B. 5 kHz
 - C. 30.24 kHz
 - D. 15 kHz
 - f) Convert the following nos
 $(11011.101)_2 = (\quad)_{10}$
 $(436)_8 = (\quad)_{16}$
 - g) Which IC is used for the implementation of 1-to-16 DEMUX?
 - A. IC 74154
 - B. IC 74155
 - C. IC 74139
 - D. IC 74138
 - h) How many 3-line-to-8-line decoders are required for a 1-of-32 decoder?
 - A. 1
 - B. 2
 - C. 4
 - D. 8
 - i) The output of AND gate will be 1 only when all of its inputs are equal to _____
 - j) The storage element for a static RAM is the _____.
 - A. diode
 - B. resistor
 - C. capacitor
 - D. flip-flop

- Q2 Answer the following questions: *Short answer type* (2 x 10)**
- a) Find the 2s complement of the following binary numbers:
A. 101110
B. 110011.11
 - b) Perform following subtraction using 2's complement method
 $(11010)_2 - (10000)_2$
 - c) What is shift register? Draw the circuit diagram for it.
 - d) What is state diagram?
 - e) Design a 3 bit binary down counter.
 - f) Differentiate between volatile and non-volatile memory.
 - g) Implement EXOR function using NAND gates only.
 - h) What is a Latch?
 - i) Express the Boolean function $F = AB + A'C$ in a product of maxterm
 - j) What is tri state logic? Where it is used. Explain.

Part – B (Answer any four questions)

- Q3**
- a) Design a combinational circuit which acts as a both full adder and full subtractor. (10)
 - b) Implement the following boolean function using single 8:1 multiplexer (5)
 $F(A,B,C,D) = \sum m(1,4,6,9,13)$
- Q4**
- a) Explain working of master-slave JK flip-flop with necessary logic diagram, state equation and state diagram. (10)
 - b) List few comparison of Combinational logic circuit and sequential Logic Circuit (5)
- Q5**
- a) Given the Boolean function: (10)
 $XY + XY + YZ$
Implement it
(i) with OR and NOT gates.
(ii) with AND and NOT gates
 - b) Write short notes on RAM and ROM. (5)
- Q6**
- a) Design a combinatorial circuit that converts a decimal digit from 2,4,2,1 code to the 8,4,2,1 code? (10)
 - b) Compare SRAM, DRAM in terms of cost, size, packing density, speed and technology. (5)
- Q7**
- a) Define Mealy machine and explain with an example. Define Moore machine and explain with an example (10)
 - b) Design a 3 bit asynchronous counter using SR flip flop. (5)
- Q8**
- a) Design the MOD-8 ripple counter. (10)
 - b) Explain with a neat diagram of a Ring counter. (5)
- Q9**
- a) Design a Mealy type sequence detector to detect a serial input sequence of 101. (10)
 - b) Explain the concept or terms: fan in, fan out, power dissipation. (5)