

Registration no:

--	--	--	--	--	--	--	--	--	--

**Total Number of Pages: 02**

bput question papers visit <http://www.bputonline.com>

**M.Sc.I  
FPYC402**

**4<sup>th</sup> Semester Regular Examination – 2016-17**

**ELECTRONICS**

**BRANCH(S): M.Sc.I(AP), M.Sc.I(AP)**

**Time: 3 Hours**

**Max Marks: 70**

**Q.CODE:Z755**

**Answer Question No.1 which is compulsory and any five from the rest.  
The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions:** (2 x 10)
- a) Distinguish between p- type and n- type semiconductor.
  - b) What is a zener diode.
  - c) What are the limitations of h –parameters ?
  - d) Define band width.
  - e) What is NAND gate ?
  - f) Calculate  $I_E$  in a transistor for which  $\beta = 50$  and  $I_B = 20 \mu A$  .
  - g) What do you mean by class A, class B and class- C power amplifiers ?
  - h) Write the difference between positive and negative feedback .
  - i) A carrier of 100 V and 1200 kHz is modulated by a 50 V, 1000 Hz sine wave signal. Find th modulation factor.
  - j) What is demodulation?
- Q2**
- a) Explain the working of a half wave rectifier and derive expressions for efficiency and ripple factor. (6)
  - b) A half – wave rectifier is used to supply 50 V d.c to a resistive load of 800 ohm. The diode has a resistance of 25 ohm. Calculate a.c. voltage required. (4)  
bput question papers visit <http://www.bputonline.com>
- Q3**
- a) Draw the equivalent circuit of an ideal zener in the breakdown region. And explain how zener diode maintains constant voltage across the load. (6)
  - b) Describe the action of L – section filter. (4)
- Q4**
- a) Draw the input and output characteristics of transistor in CB configuration. Also explain how you will draw d.c. load line of a transistor. (6)
  - b) The Q – point parameters for a transistor are  $I_C = 5.202 \text{ mA}$  ,  $I_{CO} = 2 \mu A$  ,  $I_B = 50 \mu A$ . Find  $\alpha$ ,  $\beta$  and  $I_E$  . Also find what value of base current will make  $I_C = 8 \text{ mA}$ . (4)

bput question papers visit <http://www.bputonline.com>

- Q5 a) Explain with a neat diagram the operation of push – pull amplifier circuit. (5)  
b) What do you understand by hybrid parameters? Find out them and also write about their dimensions. (5)
- Q6 a) Draw the circuit diagram of two stages R-C coupled amplifier. Derive an expression for its voltage gain in the mid-frequency and low frequency regions (5)  
b) Discuss with a neat circuit diagram the operation of a N – channel JFET. Draw the output characteristics curve of JFET. (5)
- Q7 a) .Write down the criterion for sustained oscillation. Draw a neat diagram for Hartley oscillator and explain its operation. (6)  
b) The overall gain of a multistage amplifier is 140. When negative voltage feedback is applied, the gain is reduced to 17.5. Find the fraction of the output that is feedback to the input. (4)
- Q8 a) What do you mean by modulation? Distinguish between amplitude modulation and frequency modulation. (6)  
b) Explain OR function with a 2- input OR gate. (4)

bput question papers visit <http://www.bputonline.com>