

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 01

M.Sc.I
FPYE206

2nd Semester Back Examination 2018-19

PHYSICS-II

BRANCH : M.Sc.I(AC)

Time : 3 Hours

Max Marks : 70

Q.CODE : F367

Answer Question No.1 which is compulsory and any five from the rest.

The figures in the right hand margin indicate marks.

- Q1 Answer the following questions : (2 x 10)**
- a) What is vector triple product?
 - b) State Gauss' law in electrostatics.
 - c) What are dielectrics? Define dielectric constant.
 - d) State Biot and Savart's law.
 - e) Give the physical significance four Maxwell's equations.
 - f) What is Q-factor?
 - g) What is half wave rectifier?
 - h) How does RC coupled amplifier work? Give its advantage.
 - i) What is Colpitt's oscillator?
 - j) Give the necessary criteria for maintenance of sustained oscillation in an electronic oscillator.
- Q2 a) State and prove Stokes theorem. (5)**
b) Deduce the differential form of Gauss law. (5)
- Q3 a) Using Biot and Savart's law, find the magnetic field due to a straight conductor of infinite length carrying current in a perpendicular distance from the conductor. (5)**
b) State and prove Ampere's circuital law. (5)
- Q4 a) Find an expression for the decay of current in a circuit containing an inductance and a resistance. (5)**
b) Find an expression for power in an AC circuit. (5)
- Q5 a) Draw the circuit diagram and explain the working of a full wave rectifier. (5)**
b) Explain the principle of demodulation function and basic theory of linear diode detectors. (5)
- Q6 Determine the electric field of charges uniformly distributed over an infinite plane surface and spherically symmetric charge distribution using Gauss theorem. (10)**
- Q7 Obtain an expression for the growth and decay current in RC circuits. (10)**
- Q8 Write short answer on any TWO : (5 x 2)**
- a) Gauss divergence theorem
 - b) Decay current in RC circuit
 - c) Hartley Oscillator