

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

M.Tech
PSPE101

1st Semester Back Examination 2019-20

ADVANCED POWER ELECTRONICS

BRANCH : ELECTRICAL ENGG., POWER AND ENERGY ENGG, POWER ENGG AND
ENERGY SYSTEMS

Max Marks : 70

Time : 3 Hours

Q.CODE : HB871

Answer Question No.1 which is compulsory and any FIVE from the rest.

The figures in the right hand margin indicate marks.

- Q1 Answer the following questions : (2 x 10)**
- a) Why we go for SMPS instead of phase-controlled rectifier for controlled DC supply?
 - b) Why electrical isolation is required in switch mode DC power supply ?
 - c) What is the input output voltage relationship of cuk converter ?
 - d) What are the merits of three level inverter over two level inverter ?
 - e) How sinusoidal-pulse modulation techniques work ?
 - f) What is zero crossing detector and why is it utilized in a triggering circuit ?
 - g) What is the role of energy storage components in the grid connected renewable energy generation system ?
 - h) What is the advantage of High voltage DC Transmission ?
 - i) Draw the V-I characteristics for switched mode converter versus zero-voltage/zero-current switching.
 - j) What is the maximum line voltage you will get at the output of 3 phase Voltage Source Inverter controlled by Sin PWM technique, if its input DC link voltage is 400 V ?
- Q2 a) Explain current mode controlled flyback regulator. (5)**
- b) Explain resonant AC power supply. (5)**
- Q3 a) What are the elements of SMPS ? Discuss its advantages and disadvantages. (5)**
- b) Discuss the operation of switch mode DC power supplies. (5)**
- Q4 a) Draw and explain the control circuit block diagram for a cycloconverter with non-circulating current mode. (5)**
- b) The 2cs resonant converter deliver maximum power of $w/P_L = 400\text{mw}$ at $v_o = 4\text{v}$ the supply voltage $V_s = 12\text{v}$. The maximum operating frequency 50Hz. Determine the value of L and C assume t_1 and t_3 are very small and $x = 1.5$. (5)**
- Q5 a) What is the conditioning of power factor? Discuss multistage converter used for conditioning of power factor. (5)**
- b) A single phase 220V, 1KW electric room heater is connected across 220V power supply through a TRIAC. For a delay angle of 90° , calculate the power dissipated by the heater element. (5)**

- Q6** With the help of neat circuitry and waveform, explain the operation of forward converter with tertiary winding. Also test the advantage and disadvantage of the same. **(10)**
- Q7** Explain the three phase full wave controller with star connected resistive load also draw wave forms. **(10)**
- Q8** **Write short answer on any TWO :** **(5 x 2)**
- a) Bi-directional AC power supply
 - b) Full bridge converter
 - c) M type ZCS resonant.