

Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

M.Tech
P1ELBC04

1st Semester Regular Examination 2017-18
INTEGRATED CIRCUIT DESIGN
BRANCH : ELECTRICAL AND ELECTRO ENGG

Time : 3 Hours

Max Marks : 100

Q.CODE : B1013

Answer Question No.1 which is compulsory and any FOUR from the rest.
The figures in the right hand margin indicate marks.

Assume values wherever missing

- Q1 Answer the following questions: (2 x 10)**
- Show graphically that as the bias current, I_{bias} , decreases in an active load inverter, the gain increases for some time and then it becomes independent of I_{bias} .
 - Draw the circuit of a cascode with cascode load.
 - Implement a SR Latch using CMOS.
 - What are Mixed Signal Systems? What is an ATE?
 - What is HEMT? Mention one of its applications.
 - What is ATE? What are its main components?
 - Draw the layout diagram for the CMOS logic implementation for the given logical function $Q = \overline{AB(CD + CE) + F}$.
 - Implement a SRAM cell using CMOS logic.
 - Why PMOS is used as pull up network and NMOS as pull down network?
 - What is voltage reference circuit? Write down different techniques used in reference circuits?
- Q2 a) (i) For a CMOS inverter with the following parameters: $V_{DD} = 3V, V_{tn} = 0.6V, V_{tp} = -0.82V, k' = 100\mu A/V^2, \mu_n = 2.2\mu_p$: Determine the beta ratio, β_n/β_p , for a midpoint (switching threshold) of $V = 1.3V$. Also determine the relative device widths, W_p/W_n , for $V = 1.3V$. (10)**
- (ii) A pMOS transistor of $W=3\mu m$ and $L=0.6\mu m$ has parameters $t_{ox}=500nm$, surface mobility $\mu_p = 200 cm^2/V - sec$ and threshold voltage $V_{tp} = -0.6V$. $V_{DD} = 3V$. Calculate the transistor transconductance, β_p . Also estimate the channel resistance, R_p , at $V_{SG}=V_{DD}$.
- b) Define Noise Margins. Derive the Noise Margin for a symmetrical CMOS Inverter. (10)**
- Q3 a) Calculate the input and output impedance of a Source Follower. (10)**
- b) Find the voltage gain of the common-source amplifier of Figure Q3 (b) with $V_{DD} = 5V, R_D = 5k\Omega, k' = \mu_n C_{ox} = 100\mu A/V^2, W = 50\mu m, L = 1\mu m, V_t = 0.8V, L_d = 0, X_d = 0$, and $\lambda = 0$. Assume that the bias value of V_i is 1 V. (10)**

 


Figure Q3 (b)

- Q4** a) Explain the concept of Dynamic gate? Explain with an example. What are the issues in Dynamic Design? (10)
b) Discuss different types of Current Mirror Circuits. (10)
- Q5** a) Explain datasheets? Explain the different components of test program (10)
b) Define line regulation, load regulation, input impedance, and output impedance? Explain DC gain measurement? (10)
- Q6** a) What is FinFET? Discuss its construction and uses. (10)
b) Write short notes on Floating gate MOS and Organic FET? (10)
- Q7** a) For a Cascode Amplifier, draw its small signal equivalent and give the value of its V_{bias} . Also calculate its gain. (10)
b) How will IC Design impact Internet of Everything? (10)