

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 02

M.Tech.
P2PDCC01

2nd Semester Regular / Back Examination 2017-18
ADVANCED POWER CONVERTER
BRANCH : ELECTRICAL AND ELECTRO ENGG,
POWER ELECTRO, POWER ELECTRO & DRIVES, POWER ELECTRO AND
ELECTRICAL DRIVES, POWER ELECTRO AND POWER SYSTEMS

Time : 3 Hours

Max Marks : 100

Q.CODE : C640

Answer Question No.1 which is compulsory and any FOUR from the rest.

The figures in the right hand margin indicate marks.

Answer all parts of a question at a place.

- Q1** Answer the following questions: *Short answer type* : (2 x 10)
- a) What is the difference between 180 degree and 120 degree conduction three phase bridge Inverter? Write the expression for the phase voltage in both the conduction mode.
 - b) What is the difference between Harmonic Factor and Total Harmonic Distortion?
 - c) Write the advantages of cascaded multilevel inverter.
 - d) What do you understand by Null Vector in Space Vector Modulation technique?
 - e) Explain in brief, how forward converter is better than flyback converter?
 - f) How does the quality of the output voltage waveform effects, if a step-down DC-DC converter is operated with a switching frequency of 50Hz?
 - g) Draw the various switching configuration for Zero Voltage Switching resonant converter.
 - h) The transformer utilization factor of a rectifier is 0.286. Determine the rating of the transformer required to deliver 10W dc power to the load.
 - i) Three phase half wave rectifier is connected to a resistive load, where the conduction angle of each diode is $2\pi/3$. Draw the waveform of the (i) voltage across resistive load (ii) current through diode in any one phase.
 - j) In the Sinusoidal Pulse Width Modulation technique, what is the significance of modulating frequency in bipolar and unipolar switching?
- Q2** a) Draw the circuit diagram for a fly back converter, switch mode DC power supply. Also draw the waveform of the current through load and the voltage across the switch. (10)
- b) Write a shot note on two-level Space Vector Modulation and obtain the voltage vector for different switching states. (10)
- Q3** a) Derive the expression for the current in a step up DC-DC converter feed to a resistive load. (10)
- b) Explain the working of Cuk regulator with the help of suitable circuit diagram. (10)
- Q4** a) A single-phase bridge-rectifier is supplied from a 220V, 50Hz source. The load resistance is $R=500\Omega$. (a) Design a C filter so that the ripple factor of the output voltage is less than 5%, (b) With the value of capacitor C in part(a), calculate the average load voltage V_{dc} . (10)
- b) With the help of suitable circuit diagram, explain the working of single phase dual converter. (10)

- Q5** a) A 3-level Cascaded Multilevel Inverter is used to generate 7-level output voltage waveform. Obtain the Fourier series expression of the output voltage waveform. (10)
- b) Draw the circuit diagram of a modified 5-level diode-clamped inverter with distributed clamping diode. And explain the forward path and free-wheeling path for any two levels. (10)
- Q6** a) Derive the Fourier series expression of the output voltage for a Half-Wave Rectifier. (10)
- b) A battery of 12V is charged from a Half-wave rectifier circuit, its capacity is 100Wh. The average charging current should be $I_{dc}=5A$. The input voltage is 60V, 50Hz. Calculate (a) The conduction angle of the diode, (b) the current limiting resistance R, (c) The power rating P_R of R. (10)
- Q7** a) Draw a suitable diagram for M-type Zero Current Switching (ZCS) resonant converter. And obtained the waveform of the current through inductor and voltage across capacitor. (10)
- b) Explain in brief the various modes of operations in M-type ZCS resonant converter. (10)