

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Page : 01

M.Tech
PPPE201

2nd Semester Back Examination 2017-18
HVDC & FACTS
BRANCH : POWER ELECTRO AND POWER SYSTEMS
Time : 3 Hours
Max Marks : 70
Q.CODE : C1095

Answer Question No.1 which is compulsory and any five from the rest.
The figures in the right hand margin indicate marks.

Answer all parts of a question at a place.

- Q1 Answer the following questions : (2 x 10)**
- a) Show the variation of voltage along the line with load for HVDC Transmission and ac transmission.
 - b) What is surge impedance loading?
 - c) Give the equivalent circuit of the inverter based on the angle of advance (β).
 - d) Explain about Voltage Dependent Current Order Limit.
 - e) What are the different types of MTDC systems used?
 - f) Compare single phase ac line with monopolar dc line for power transfer capability.
 - g) Injecting voltage in series with the line can provide a powerful means of controlling the active and reactive power flow. Justify.
 - h) What are different categories of FACTS controllers?
 - i) What is sub synchronous resonance?
 - j) Give the amplitude variation of the fundamental TCR current with delay angle α .
- Q2 a) What are different components of HVDC system? Explain the purpose of each. (5)**
b) Compare the insulation level of a bipolar DC line with three phase AC line for same power transmission and equal losses. (5)
- Q3 Describe Two and Three valve operation mode of a three phase Converter with delay angle α and overlap angle μ . (10)**
- Q4 Shows that the harmonics contain in the current waveforms of converter transformer are of the order $np \pm 1$. (10)**
- Q5 a) Explain the firing angle control for the valve in a converter. (5)**
b) What are the different type of fault occurs in a converter? (5)
- Q6 a) Derive the transfer function of SVC. (5)**
b) How series compensation helps in voltage stability. (5)
- Q7 (a) Give the operating principle of TSSC. (5)**
(b) Explain the operating control scheme for GCSC. (5)
- Q8 Write short notes on any TWO : (5 x 2)**
- a) Voltage Dependent Current Order Limit (VDCOL)
 - b) 12-pulse converter
 - c) Power oscillation damping
 - d) UPFC