

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 01

M.Tech
PPPC201

2nd Semester Back Examination 2018-19
POWER CONVERTER-II
BRANCH : POWER ELECTRO AND POWER SYSTEMS

Time : 3 Hours

Max Marks : 70

Q.CODE : F169

Answer Question No.1 which is compulsory and any FIVE from the rest.

The figures in the right hand margin indicate marks.

- Q1 Answer the following questions : (2 x 10)**
- a) What are the disadvantages of switch mode operation?
 - b) How the shortcomings of switch mode converter can be overcome?
 - c) What are the important features of diode clamped multilevel inverter?
 - d) Discuss the area of application for current regulated voltage source inverter?
 - e) Explain briefly a controlled three phase bridge rectifier with a feedback voltage control loop.
 - f) Discuss the operation of boost converter with circuit details.
 - g) What do you mean by constant switching frequency current control methods?
 - h) For a load resonant dc-dc converter, what is the disadvantage of discontinuous conduction mode with $\omega_s < \frac{1}{2}\omega_0$ as compared to continuous conduction mode with $\frac{1}{2}\omega_0 < \omega_s < \omega_0$ and $\omega_s > \omega_0$?
 - i) What are the methods of current control?
 - j) How a CSI is different from VSI?
- Q2 a) Give a comparison of single phase bridge rectifier and three phase bridge rectifier? (5)**
- b) A three phase fully controlled bridge rectifier is fed from a three phase 400 V, 50 Hz mains. For firing angle of 60° , output current is level at 20 A and output voltage is at 230 V. Calculate the load resistance, source inductance and angle of overlap? (5)**
- Q3 a) Discuss the operation of diode clamped type multilevel inverter? (5)**
- b) Explain the space vector modulation strategy? (5)**
- Q4 a) Explain the operation of buck boost SMPS topology with relevant waveforms? (5)**
- b) Explain the operation of push-pull converter? Give an example of one of its application? (5)**
- Q5 a) What are the different classifications of resonant converter? (5)**
- b) Explain the operation of class E converter? (5)**
- Q6 Discuss flyback converter and its operation both in continuous and discontinuous conduction mode? (10)**
- Q7 What is a series loaded resonant dc-dc converter? Explain its operation both in continuous and discontinuous mode of operation? (10)**
- Q8 Write short answer on any TWO : (5 x 2)**
- a) ZVS resonant switch converter
 - b) Variable band hysteresis controller
 - c) Series Inverter