

Registration No :

--	--	--	--	--	--	--	--	--	--

Total Number of Pages : 01

M.Tech  
EEPE201

**2<sup>nd</sup> Semester Back Examination 2018-19**  
**HVDC TRANSMISSION & FACTS**  
**BRANCH : POWER SYSTEM ENGG**

Time : 3 Hours

Max Marks : 70

Q.CODE : F315

**Answer Question No.1 which is compulsory and any FIVE from the rest.**  
**The figures in the right hand margin indicate marks.**

- Q1 Answer the following questions : (2 x 10)**
- State the advantages of HVDC transmission?
  - What is the function of smoothing reactor?
  - Mention two applications of DC breakers?
  - Which factors limit the transmission capacity of lines?
  - What are the advantages of IPFC over UPFC?
  - How the dynamic stability conditions affect the power flow in a power system?
  - Compare the series and shunt compensation?
  - Mention the advantages of STATCOM?
  - What is sub-synchronous resonance?
  - What are the advantages of TSC-TCR type SVC over FC-TCR type SVC?
- Q2**
- With neat diagram, explain different kinds of DC links. Explain the necessity of back to back HVDC link? (5)
  - With relevant waveform, derive the expression for average DC voltage in bridge converter with an overlap of less than 60 degree? (5)
- Q3**
- Briefly explain with neat sketch Thyristor controlled reactor (TCR)? (5)
  - What is basic principle of TCSC? Explain the different modes of operation in TCSC? (5)
- Q4**
- Describe the working principle of the two types of Static Var Compensators with schematic diagrams? (5)
  - Describe with the help of neat diagram & wave forms, the operation of 6 pulse bridge converter with delay angle  $\alpha$  and without overlap. Derive the expressions for its dc voltage stating the assumptions made. (5)
- Q5**
- With the help of 5 modes, explain the characteristics of a twelve pulse converter. (5)
  - Explain in detail about the role of SVC in enhancing the steady state power limit and power system damping? (5)
- Q6** 'Best converter circuit for HVDC transmission is 3-phase bridge'. Justify the statement by explaining the advantages of a three phase Graetz bridge configuration. (10)
- Q7** Compare HVDC and HVAC transmission for economics of operation, stability limits, voltage control and reliability. (10)
- Q8 Write short answer on any TWO : (5 x 2)**
- DC circuit breaker
  - MTDC system
  - SSSC